

mble

APPLICATION NOTE

M.B.L.E. ELECTRONICS
80, RUE DES DEUX GARES, BRUXELLES

BRY 39 APPLICATIONS

- silicon controlled switch
- thyristor tetrode
- programmable unijunction transistor


B. G. G. Couwenbergh and J. Rozenboom

129

The BRY39 is a general purpose, low power, silicon planar p-n-p-n device in a TO-72 metal envelope. The device comprises an integrated pnp-npn transistor pair of which all electrodes are accessible. Therefore many switching and logic operations requiring two or more conventional active elements can now be performed with only one BRY39.

As a four-layer device the BRY39 has the following outstanding features:

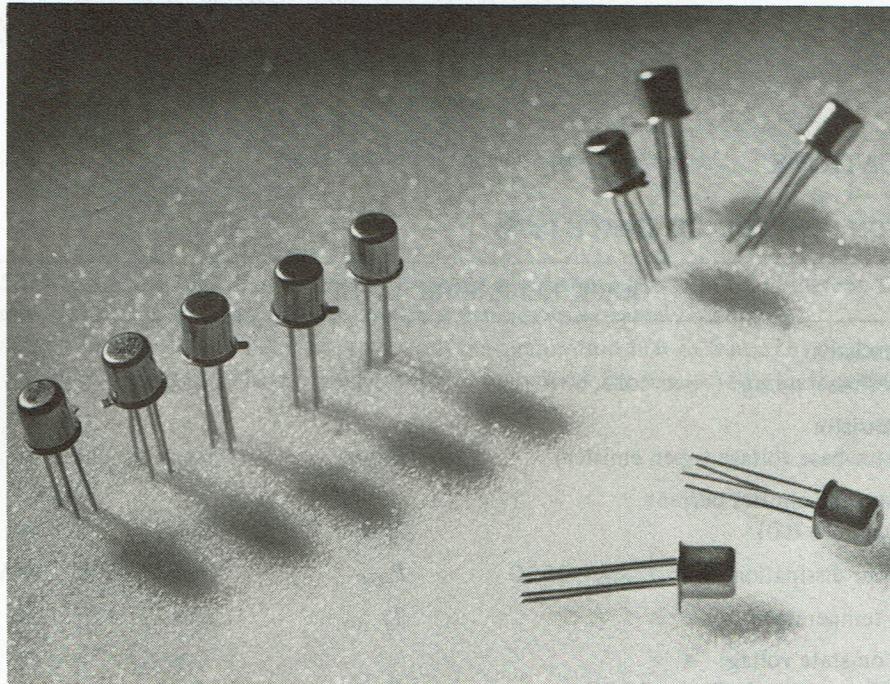- high sensitivity
- no dv/dt rate-problems
- few circuit components and hence few connections required
- low cost
- better characterization than two separate transistors.



This Application Note is furnished for guidance only, care having been taken to ensure its accuracy and completeness but no liability therefor being assumed; its publication does not imply a license under any patent, nor is it to be reproduced in any way, in whole or in part, without the written consent of the publisher.

M.B.L.E. ELECTRONICS - BRUXELLES

Fig.1 shows the schematic representation of the build-up of the layers of the p-n-p-n silicon controlled switch. Fig.2 shows that this representation can be split into an equivalent circuit comprising two interconnected transistors. Fig.3 gives the symbol for our new device, *a* stands for anode, *ag* for anode gate, *kg* for cathode gate and *k* for cathode.

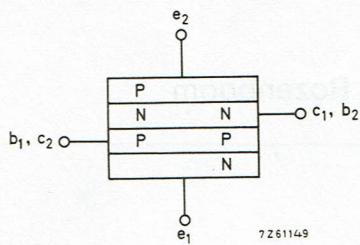


Fig.1. Schematic build-up of the p-n-p-n SCS.

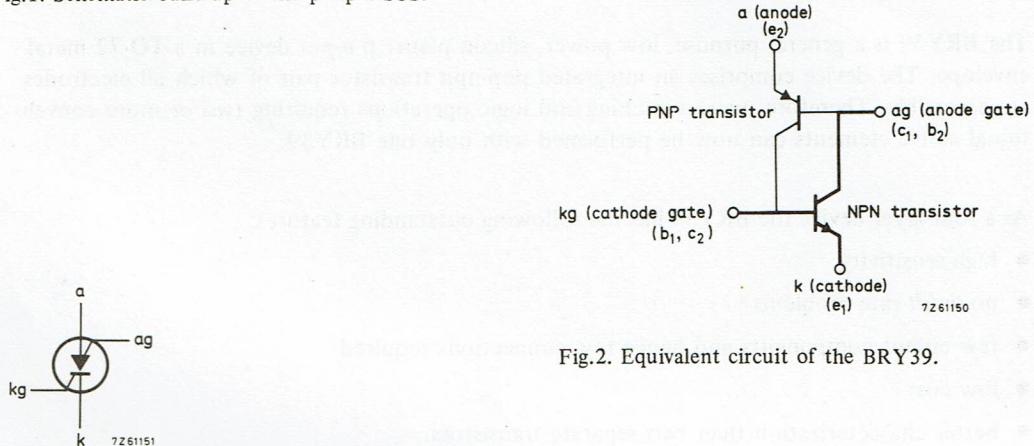


Fig.2. Equivalent circuit of the BRY39.

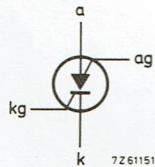


Fig.3. Symbol of the BRY39.

APPLICATIONS

1 SILICON CONTROLLED SWITCH (SCS)

QUICK REFERENCE DATA

P-N-P transistor

Emitter-base voltage (open collector) $-V_{EBO}$ max. 70 V

N-P-N transistor

Collector-base voltage (open emitter) V_{CBO} max. 70 V

Repetitive peak emitter current

$t = 10 \mu s, \delta = 0.01$ $-I_{EM}$ max. 2.5 A

Total power dissipation up to $T_{amb} = 25^\circ C$ P_{tot} max. 275 mW

Junction temperature T_j max. 150 $^\circ C$

Forward on-state voltage

$I_A = 50 \text{ mA}; I_C = 0; R_{BE} = 10 \text{ k}\Omega$ V_{AE} < 1.4 V

Holding current

$I_C = 10 \text{ mA}; -V_{BE} = 2 \text{ V}; R_{BE} = 10 \text{ k}\Omega$ I_H < 1.0 mA

Turn on time

t_{on} < 0.25 μs

turn off time

t_q < 5.0 μs

Used as an SCS the BRY39 can advantageously be used as a driver for numerical indicator tubes and in counting circuits. A decade ring-counter ($f \leq 40$ kHz) that directly drives a ZM1000 indicator tube is discussed in AI325 and AI327 (see page 7), an improved circuit being given in Fig.4. During operation ambient temperatures between 0 °C and 80 °C are allowed.

From Fig.4 it is clear that this ring-counter is simpler and less expensive than the usual design based on bistables (flip-flops). The component values have been so chosen that no stringent requirements are imposed on the amplitude and duration of the input pulses or the constancy of the supply voltages.

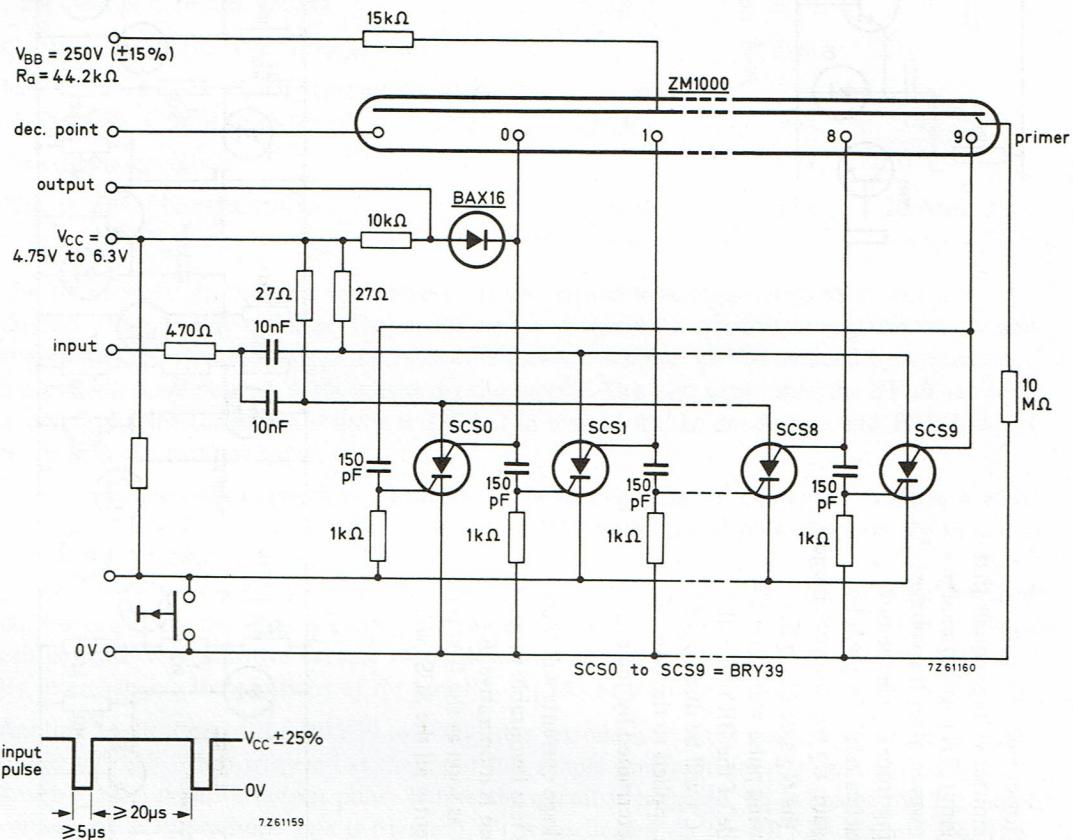


Fig.4. Decade ring-counter circuit with display.

Fig.5 shows a scaler-of-4. Six of these units are connected in cascade in Fig.6 thereby forming a capacitive scaler-of- 4^6 (time counter) which consumes an extremely low power.

To explain the working of Fig.4 we start from the assumption that SCS just has discharged C_2 and is now cut-off again. There is no input pulse present on the base of TR_1 so that this transistor

is also cut-off. C_1 is now charged to the supply voltage (D_1 connects the lower side of C_1 to earth). Since TR_2 is a silicon transistor, it is completely cut-off when its emitter voltage equals that of its base. If now a positive pulse of a certain duration is applied to the input, TR_1 will discharge C_1 so that only the saturation voltage of TR_1 is left across C_1 . This is, however, after the voltage drop at the diode side of C_1 has been cancelled by a charge current flowing from C_2 via the now conducting transistor TR_2 into C_1 . As soon as the emitter of TR_2 approaches zero, TR_2 will be cut-off again. If now the input pulse ceases to exist, C_1 will be charged again. C_2 will thus be charged by an amount necessary to discharge C_1 and consequently the voltage at the R_2 side of C_2 has dropped correspondingly (neglecting the base circuit of TR_2). Any following pulse will cause C_2 to gain the same charge until at the fourth pulse the voltage at the cathode of the BRY39 will fall below the cathode gate voltage, thus causing the BRY39 to conduct. C_2 will be discharged again and the cathode gate of the BRY39 rises, so that a positive pulse is applied to the base of TR_3 (input stage of the next scaler-of-4). The division factor is mainly determined by the ratio between C_1 and C_2 .

At too low a counting rate the circuit will not work properly because leakage currents will then charge and discharge the capacitors. Deliberate use has been made of this less favourable property by providing an extra leakage path via R_2 . During the time that the system is inoperative, R_2 discharges C_2 to such an extent that the SCS is just not switched on. But as soon as the first pulse is applied to the input of the scaler-of-4⁶ of Fig. 6, the first, and consequently all the SCSs will discharge, so that the entire counter is reset.

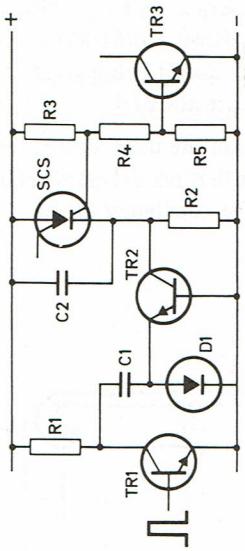


Fig. 5. Low power scaler-of-4.

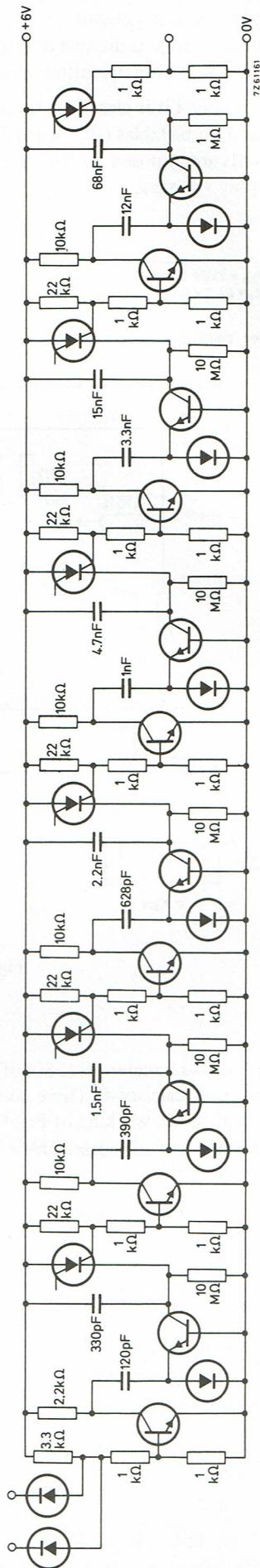


Fig. 6. Capacitive scaler-of-4⁶. Silicon controlled switches: BRY39; transistors: BCY39; diodes: BAX13. Supply voltage between 4.1 V and 7.9 V; ambient temperature from 20°C to 80°C.

2 THYRISTOR TETRODE

QUICK REFERENCE DATA

Continuous off-stage voltage	V_D	max.	70 V
Continuous reverse voltage	V_R	max.	70 V
Repetitive peak off-state voltage	V_{DRM}	max.	70 V
Repetitive peak reverse voltage	V_{RRM}	max.	70 V
On-state current (d.c.) up to $T_{case} = 85^\circ\text{C}$	I_T	max.	250 mA
Non-repetitive peak on-state current $t = 10 \mu\text{s}$; $T_j = 150^\circ\text{C}$ prior to surge	I_{TSM}	max.	3 A
Junction temperature	T_j	max.	150 °C
Rate of rise of on-state current	dI_T/dt	max.	20 A/ μs

The BRY39 can also be used as a small thyristor tetrode in sensing networks in which it directly drives a relay or lamp. The circuit can be designed for positive or negative supply and trigger voltages. Spurious triggering caused by unwanted pulses can be avoided by connecting the gate, that is not used, via a resistor to the supply. This also diminishes the dV/dt sensitivity. A practical value for such a resistor is 220 kΩ in series with the anode gate and 10 kΩ in series with the cathode gate.

Fig.7 shows a sensing network in which R_1 is the sensing element, chosen in accordance with the light, temperature, or radiation to be sensed. The resistance of potentiometer R_2 should be of the same magnitude as that of R_1 .

In the arrangement shown, a decline in the resistance of R_1 causes the BRY39 to be switched on. Consequently the relay is closed, thereby activating a warning system. This sensing network can be made very sensitive because of the low current that is required to trigger the BRY39. By interchanging the positions of R_1 and R_2 , R_1 has to increase for triggering the alarm.

Another application of the BRY39 as a thyristor tetrode is in a complementary pulse generator shown in Fig.8. When triggered at the input this simple generator delivers simultaneously a positive and a negative output pulse. Before the circuit is triggered, C_1 is charged to the supply voltage. After the cathode gate is triggered, C_1 is discharged via the BRY39, R_4 and R_5 . The amplitude of the pulses is about half the supply voltage. The values of R_3 , R_5 and C_1 determine the current and pulse width. When C_1 is discharged the BRY39 ceases to conduct because R_3 keeps the anode current below the holding current of the BRY39. The capacitor C_1 is now charged again after which the circuit can be triggered again.

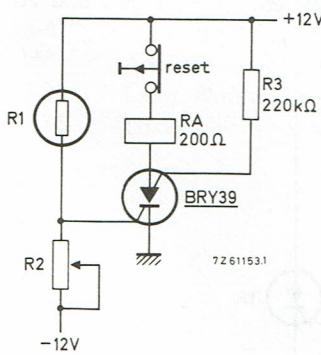


Fig.7. Sensing network. R_3 decreases the dV/dt rate and the input sensitivity.

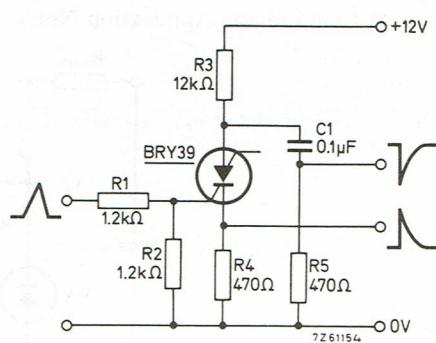


Fig.8. Monostable circuit for generating complementary output pulses.

3 PROGRAMMABLE UNIJUNCTION TRANSISTOR (PUT)

QUICK REFERENCE DATA

Anode gate-cathode forward voltage	V_{FAGK}	max.	70 V
Anode gate-anode forward voltage	V_{FAGA}	max.	70 V
Anode current (d.c.) up to $T_{case} = 85^\circ\text{C}$	I_T	max.	250 mA
Junction temperature	T_j	max.	150 °C
Peak current $R_G = 10 \text{ k}\Omega$; $V_S = 10 \text{ V}$	I_P	max.	5 μA
Valley current $R_G = 10 \text{ k}\Omega$; $V_S = 10 \text{ V}$	I_V	>	70 μA

As a programmable unijunction transistor the BRY39 can be used in circuits for motor control (phase controlled) oscillators, timers, pulse shapers, trigger devices, etc. The PUT can also be used instead of a relay.

Although the construction of the BRY39 differs much from that of a unijunction transistor, it can be used as such. It is then called programmable unijunction transistor (PUT) because the values for I_P , I_V and V_S , which are fixed for a common unijunction transistor, may be chosen freely, provided the values of the bias resistors are chosen appropriately.

Fig.9 shows a trigger circuit for power control with the aid of a thyristor. Fig.10 shows the pulse height V_O that can be obtained at a certain supply voltage V_S for two different values of C .

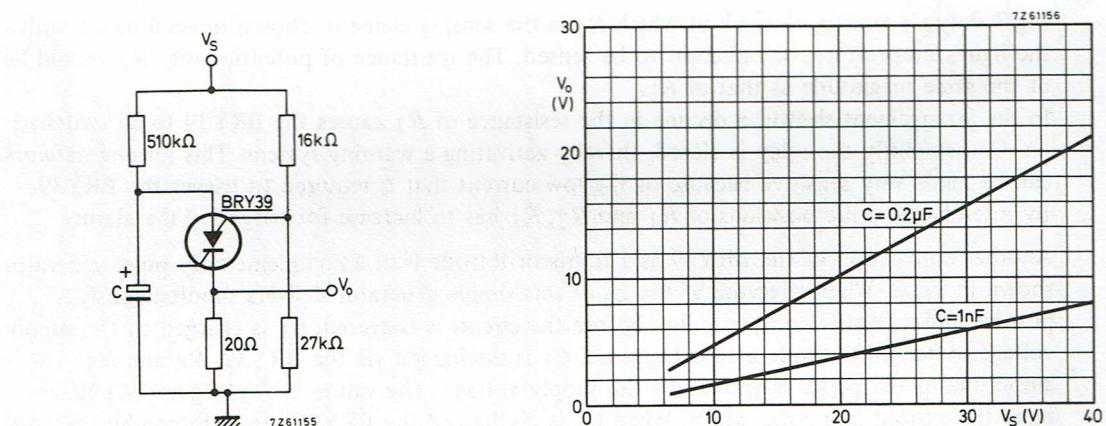


Fig.9. Trigger circuit for high energy trigger pulses.

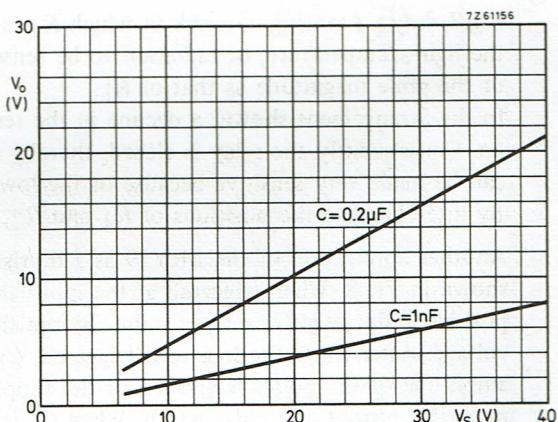


Fig.10. Pulse amplitude versus supply voltage with C as a parameter for the circuit of Fig.9.

Thanks to the thyristor action of the BRY39 the risetime of the pulse is very short (80 ns).

Fig.11 shows a complete circuit for power control. Details about the circuits of Figs 9 and 10 can be found in the Application Notes AN80 and AN82.

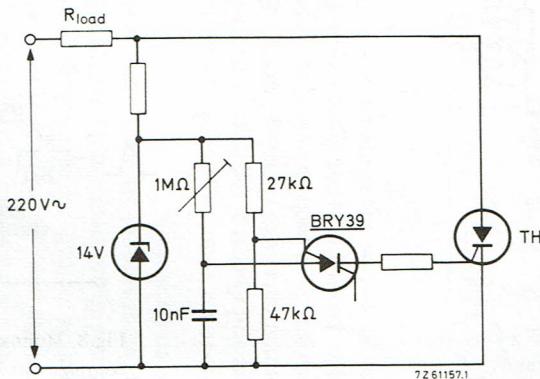


Fig.11. Complete circuit for power control.

Fig.12 shows a relaxation oscillator which can be used for triggering a thyristor. A constant anode gate voltage is provided by voltage divider R_3 , R_4 . If we start from the situation that C has just been discharged and BRY39 is cut-off again, C will be charged via R_1 . As soon as the voltage across C is high enough (V_P), BRY39 will switch on, provided the current flowing in the anode is high enough (I_P). As a result C will be discharged, after which the holding current (I_V), necessary for the BRY39 to stay switched-on, cannot be provided by R_1 , so that BRY39 is switched-off again. Diode D is used to compensate variations in V_P (depending on anode-anode gate voltage) due to ambient temperature variations or warming-up of the device (D should always be at the same temperature as BRY39). Best results are obtained by making I_D at the switch-on moment of BRY39 equal to I_P .

More information about the BRY39 used as a PUT can be found in the data sheets.

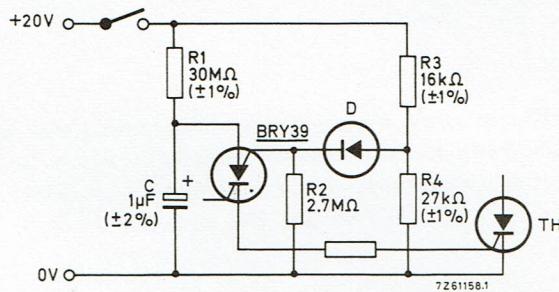


Fig.12. Relaxation oscillator for triggering SCR.

AVAILABLE PUBLICATIONS:

Application Informations:

- 325 Circuit logic with silicon controlled switches.
- 327 Cold cathode numerical indicator tubes, operating principle, behaviour and applications

Application Notes:

- 41 Thyristor trigger circuits
- 64 Pulse triggering of thyristors and triacs with BRY39 silicon controlled switch
- 80 A.C. fan motor control
- 82 Lamp dimmer
- 115 Timer unit for single-phase welding systems using 50-series circuit blocks

un anti-vol réellement efficace...

Le circuit proposé ici peut protéger aussi bien votre porte de rue ou d'appartement que votre voiture. Il décourage les malfaiteurs les plus ingénieurs.

Son principe est simple, le système constitue en fait un verrou électronique commandé par un clavier à neuf touches.

Le déblocage ne se réalise que si l'on forme un code préétabli par le propriétaire et cela dans un temps assez court.

Ce système empêche aussi toute personne en état d'ébriété de prendre le volant.

Dans ce cas en effet, les réactions sont généralement lentes et le conducteur ne pourra pas former le code dans le temps voulu.

DESCRIPTION DU SYSTEME

La figure 1a donne le schéma-bloc d'un système alimenté par batterie, la figure 1b donne la version alimentation secteur.

Il faut noter que dans le cas d'une alimentation par secteur, la source de tension pour le relais ou la serrure doit être séparée de celle pour le circuit électronique.

Le système anti-vol se compose essentiellement d'une unité de commande à neuf boutons-poussoirs et d'une unité de contrôle.

La figure 2 donne le schéma électrique du système. La commande du relais ou de la serrure se fait par quatre commutateurs électriques SCS (« Silicon controlled switch ») du type BRY 39 ou BR 101 (TH 1 à TH 4).

La gâchette de cathode de chaque commutateur est reliée à l'un des boutons-poussoirs, le choix de ceux-ci est tout à fait arbitraire et détermine le code à respecter pour déverrouiller le système. Les quatre

commutateurs sont reliés en série et ne conduisent que si la gâchette de cathode est positive et si l'anode est déjà positive.

En d'autres termes, l'anode ne sera positive que si le commutateur précédent conduit (sauf pour TH 1). TH 1 doit donc conduire avant TH 2, TH 2 avant TH 3 et TH 3 avant TH 4. Il y a donc également une séquence à respecter dans la combinaison des 4 chiffres du code.

Lorsqu'on enonce le bouton-poussoir raccordé à TH 1, ce dernier conduit et l'anode de TH 2 devient positive. TH 2 peut conduire si l'on enonce le bouton-poussoir correspondant, de même pour TH 3 et TH 4.

Lorsque les quatre commutateurs conduisent, la cathode de TH 4 reliée à la base du transistor TR 1 (via R 14) devient positive.

TR 1 et TR 2 conduisent et le courant est suffisant pour actionner un relais ou une serrure.

L'échelon de tension fourni par l'enfoncement d'un bouton-poussoir correspondant au code est « différentié » par un des condensateurs C2 - C4 - C6. L'impulsion positive qui en résulte est juste suffisante pour assurer la conduction d'un commutateur et est appliquée à la gâchette appropriée. Les condensateurs C3 - C5 - C7 et C9 dérivent les parties négatives des tensions d'interférence.


Les autres boutons-poussoirs ne correspondant pas au code sont reliés en parallèle et l'enfoncement d'un de ceux-ci ramène la gâchette d'anode de TH 1 au pôle positif de l'alimentation et le bloque. Les autres commutateurs qui seraient éventuellement conducteurs sont immédiatement bloqués par l'enfoncement d'un bouton-poussoir ne correspondant pas au code. Le code doit être alors recommencé.

Une condition pour bloquer un commutateur qui conduit consiste à rendre la gâchette d'anode plus positive que l'anode. Les diodes D1 et D2 réduisent la tension d'anode de TH 1 d'une valeur de 1,4 V par rapport à l'alimentation. Quand un bouton incorrect est enfoncé, la gâchette d'anode est ramenée à la tension positive de l'alimentation et TH 1 se bloque.

Un effet similaire est obtenu lorsque la gâchette d'anode de TH 1 est ramenée à la tension positive de l'alimentation via TR 3, nous verrons plus loin comment.

Une limitation du temps de commande est incorporée dans le circuit et débute au moment où le premier bouton-poussoir est enfoncé, c'est-à-dire lorsque TH 1 est conducteur. La cathode de TH 1 devient positive et C1 se charge à travers le potentiomètre R 17. Passé le délai préétabli par R 17, la tension de base de TR 4 devient suffisante pour que le transistor conduise. TR 3 se débloque également et TR 1 se bloque.

Si la séquence de commande dépasse le temps préétabli, le circuit retourne à son état initial. Le potentiomètre R 17 permet de varier le temps entre 0 et 8 secondes. Ce temps doit tenir compte d'une commande correcte, et du temps nécessaire pour ouvrir la porte ou actionner un relais par exemple. Aussitôt que TR 1 se bloque, C11 se décharge rapidement à travers R 3 et R 4. Si l'on supprime R 3, C11 se décharge plus lentement.

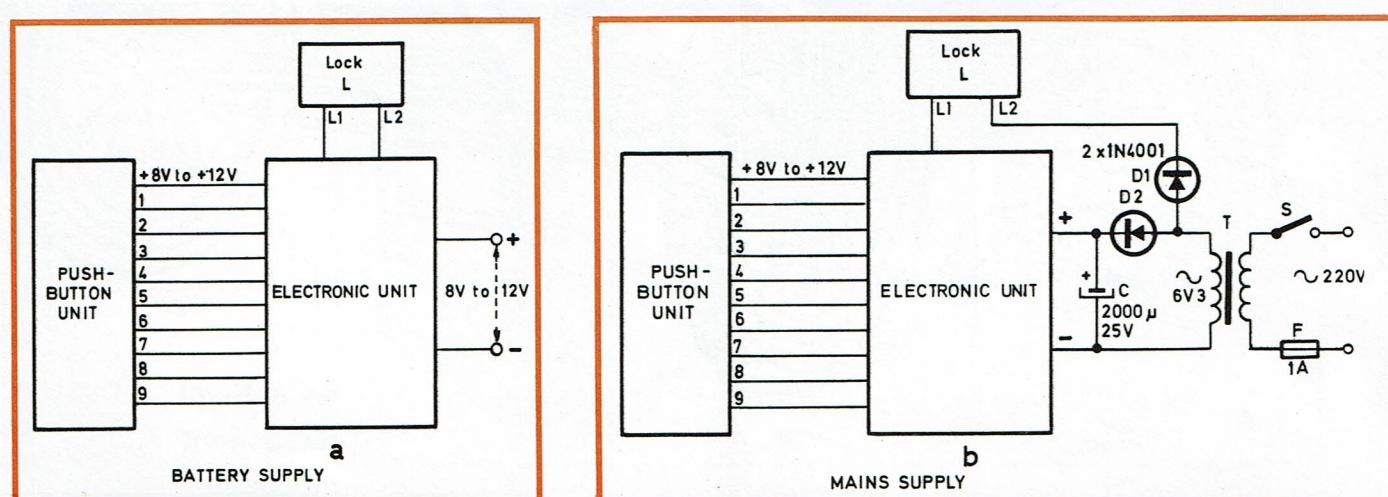

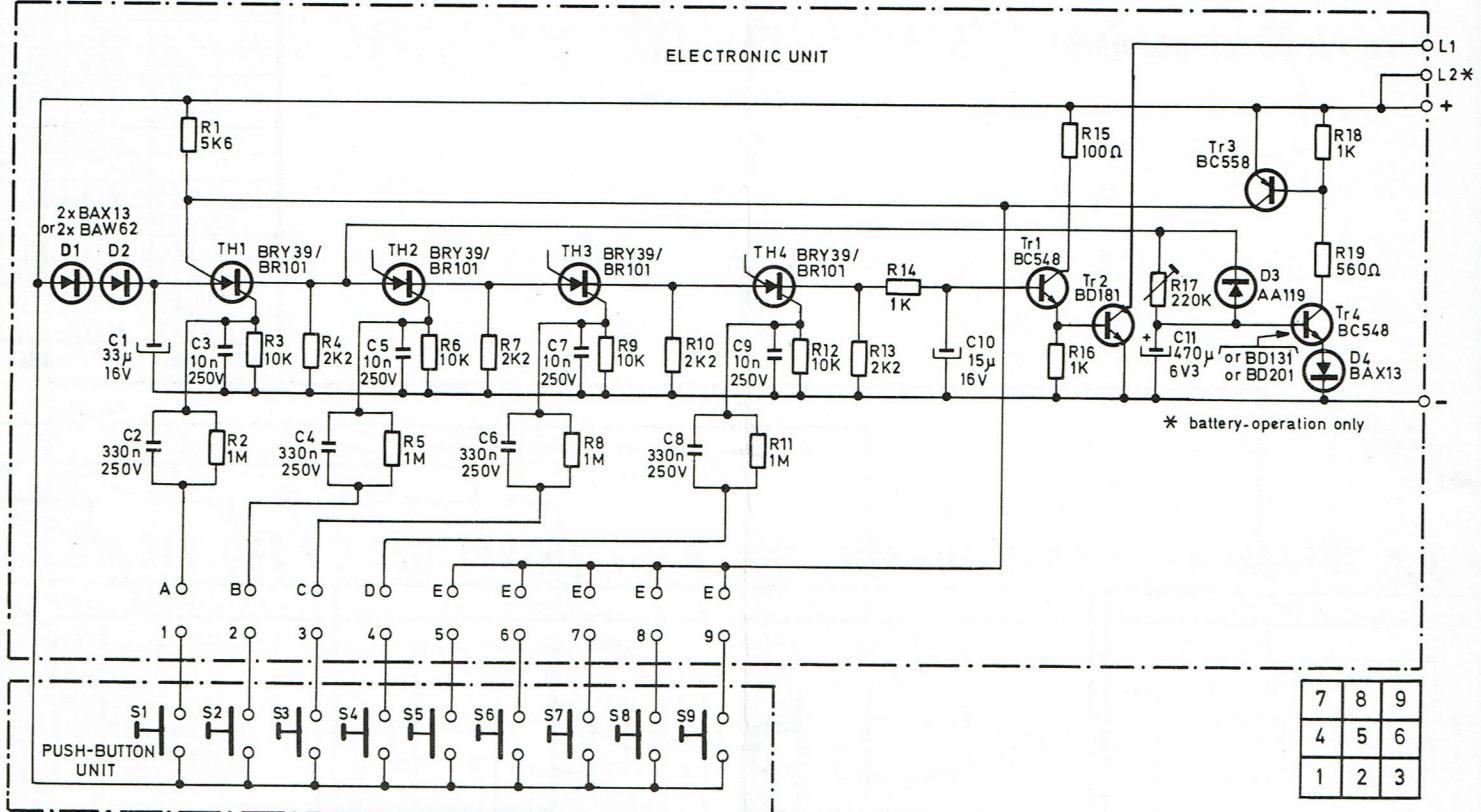


Fig. 2. Schéma électrique du système anti-vol.

ALIMENTATION

La tension d'alimentation peut varier entre 8 V et 12 V (alimentation par batterie).

Le courant consommé dépend du courant nécessaire pour actionner la serrure ou le relais. Ce courant peut varier de 0,2 A à 1 A maximum.

Dans le cas d'une alimentation secteur, un transformateur standard de 6,3 V (pour le chauffage filaments des tubes par exemple) et d'une puissance de 10 W à 20 W peut être utilisé.

UTILISATION SUR VEHICULE AUTOMOBILE

La figure 3 donne le raccordement du système dans le cas d'un antivol pour voiture.

La liaison entre clé de contact et démarreur doit être interrompue pour y insérer un relais 12 V du type relais pour phare capable de supporter un courant de 1 A.

Un interrupteur peut être mis en parallèle sur le relais pour pouvoir déconnecter le système. Pour la mise en route du moteur il suffit de suivre les opérations dans l'ordre :

1. introduire la clé de contact
2. tourner la clé en position contact
3. former le code correct
4. lorsque le code est formé, démarrer.

On peut éventuellement relier le circuit électronique directement au démarreur.

Dans ce cas, il faut choisir TR 2 en fonction du courant exigé par le relais du démarreur.

Ce système n'est toutefois pas recommandé car le démarreur pourrait continuer à tourner alors que la mise en route est déjà effective.

DETERMINATION DU CODE

Le code est préétabli par les liaisons entre les bornes 1 à 9 et A à E.

Il faut rappeler ici que le code est défini non seulement par le choix des quatre chiffres mais également par leur séquence.

Supposons par exemple qu'il existe une liaison entre :

cosses 2 et A

cosses 5 et B

cosses 0 et C

cosses 3 et D

Les cosses 1, 4, 6, 7, 8 et 9 sont raccordées à E.

Pour déverrouiller le système, il faut former la séquence 2 - 5 - 0 - 3, la séquence 2 - 0 - 5 - 0 - 3, par exemple, restera sans effet.

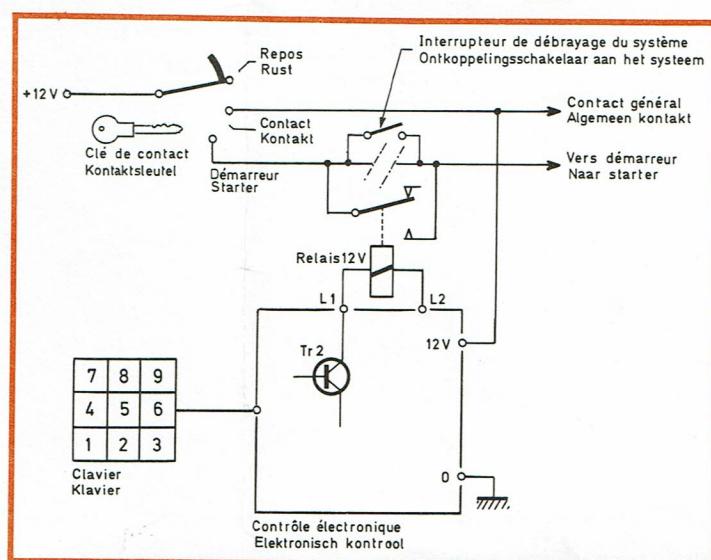


Fig. 3. Raccordement du système dans le cas d'un anti-vol pour voiture.